



**dscal**  
DIGITAL SYSTEMS & COMPUTER ARCHITECTURE LABORATORY

# Εργαστήριο Λογικής Σχεδίασης

## VHDL

**Βασιλόπουλος Διονύσης**

**Ε.Δι.Π. Τμήματος Πληροφορικής & Τηλεπικοινωνιών - ΕΚΠΑ**

# VHDL – Ακολουθιακά Κυκλώματα

## Παράδειγμα


Τι κύκλωμα μοντελοποιεί ο κώδικας;

Πως υπολογίζεται η συχνότητα λειτουργίας του κυκλώματος μετά τη σύνθεση;

```
process (clk) is
begin
  if clk'event and clk='1' then
    if reset = '1' then
      q3<='0';q1<='0';q2<='0';
    else
      q1<=a;
      q2<=b;
      q3<=q1 and q2;
    end if;
  end if;
end process;
```

# VHDL – Ακολουθιακά Κυκλώματα

## Παράδειγμα

 

# VHDL – Variables

test\_proc: process (clk) is

variable a: std\_logic;

begin

if rising\_edge(clk) then

if reset='1' then

Out\_1<='0';

else



a:=In\_1;

Out\_1<=a;

end if;

end if;

end process test\_proc;

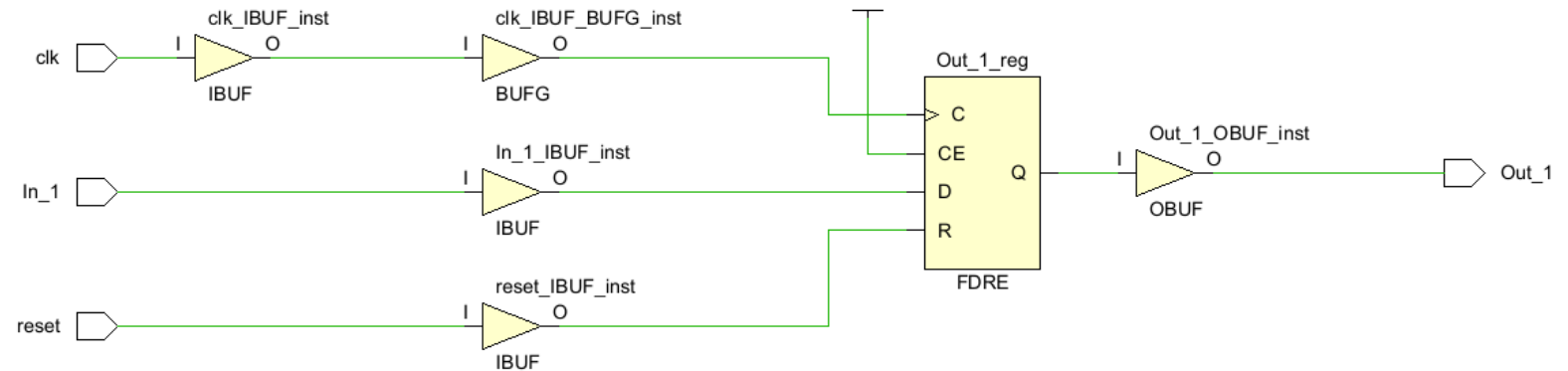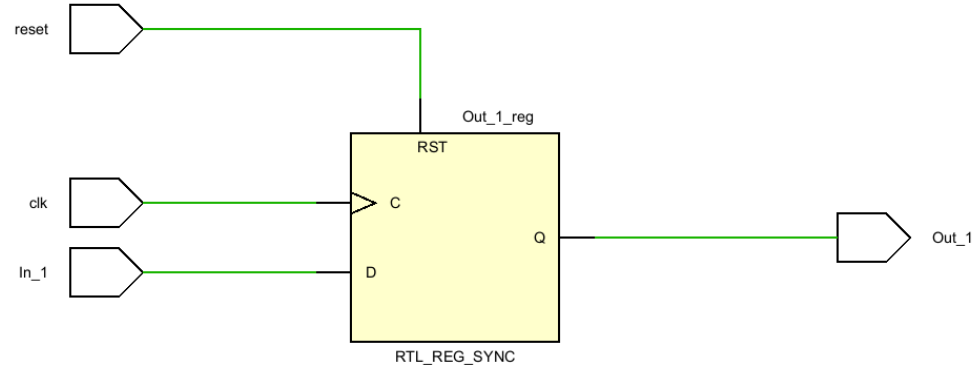

# VHDL – Variables

test\_proc: process (clk) is

variable a: std\_logic;

begin

if rising\_edge(clk) then

if reset='1' then

Out\_1<='0';

else


Out\_1<=a;

a:=In\_1;

end if;

end if;

end process test\_proc;

 

# VHDL – Assert

Ακολουθιακή και σύγχρονη εντολή (συνήθως εντός simulation)

Ελέγχει εάν μια συνθήκη είναι αληθής. Εάν ΔΕΝ είναι αληθής τότε τυπώνει ένα μήνυμα.


```
assert <condition>;  
assert <condition> severity <severity_level>;  
assert <condition> report <message_string>;  
assert <condition> report <message_string> severity <severity_level>;
```

```
condition_to_check <= true>;  
assert condition_to_check = true report "Assertion failed! Condition is false." severity error;  
  -- If the assert passes, this line will be executed  
report "Assertion passed! Condition is true." severity note;
```

Severity levels: note, warning, **error**, **failure**

```
assert i < 5 report "unexpected value. i = " & integer'image(i);
```

Scalar  
type

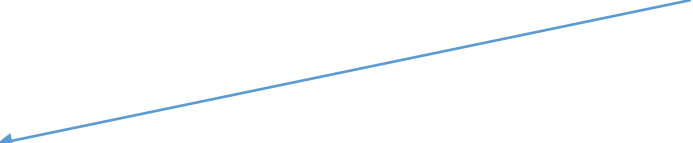


[https://peterfab.com/ref/vhdl/vhdl\\_renerta/mobile/source/vhd00007.htm](https://peterfab.com/ref/vhdl/vhdl_renerta/mobile/source/vhd00007.htm)

# VHDL – Finite State Machines

- Χρησιμοποιούνται για να υλοποιήσουν μια ακολουθία ελέγχου
- Μία FSM (Finite-State Machine – Μηχανή Πεπερασμένων καταστάσεων) ορίζεται από
  - σύνολο εισόδων:  $I$
  - σύνολο εξόδων:  $O$
  - σύνολο καταστάσεων:  $S$
  - αρχική κατάσταση:  $s_0$  ανήκει στο  $S$
  - συνάρτηση μετάβασης από μία κατάσταση στην επόμενη
  - συνάρτηση εξόδου

# VHDL – Finite State Machines

## Γενικό διάγραμμα

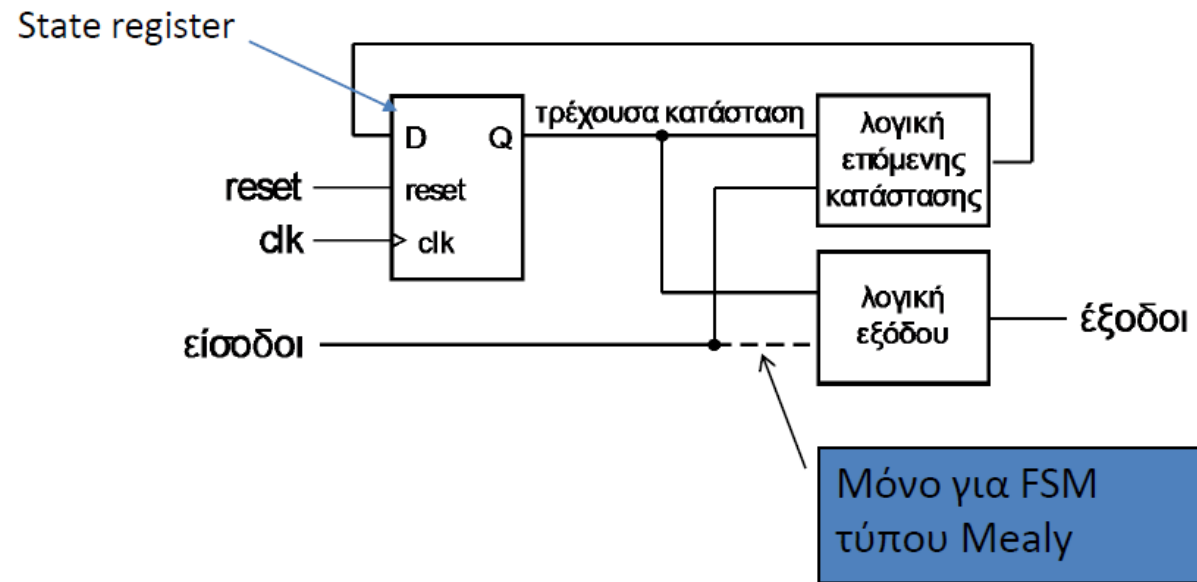



# VHDL – Finite State Machines

## Κωδικοποίηση Καταστάσεων

- Κωδικοποιούνται στο δυαδικό
  - $N$  καταστάσεις: χρειάζονται τουλάχιστον  $\log_2 N$  bit
- Η κωδικοποιημένη τιμή χρησιμοποιείται στα κυκλώματα για τις συναρτήσεις μετάβασης και εξόδου
  - η κωδικοποίηση επηρεάζει την πολυπλοκότητα του κυκλώματος
- Είναι δύσκολο να βρεθεί βέλτιστη κωδικοποίηση
  - τα εργαλεία CAD συνήθως κάνουν την κωδικοποίηση
- Η κωδικοποίηση one-hot δουλεύει καλά στα FPGA
- Συχνά χρησιμοποιείται το 000...0 για την κατάσταση αδράνειας
  - μηδενίζει τον καταχωρητή στην κατάσταση αδράνειας

# VHDL – Finite State Machines


## Κωδικοποίηση Καταστάσεων - Type

- Χρησιμοποιούμε έναν τύπο απαρίθμησης για τις τιμές των καταστάσεων
  - αφηρημένο, έτσι αποφεύγουμε να προδιαγράψουμε την κωδικοποίηση

```
type state_type is (zero, edge, one);  
signal state_reg, state_next: state_type;  
...
```

# VHDL – Finite State Machines
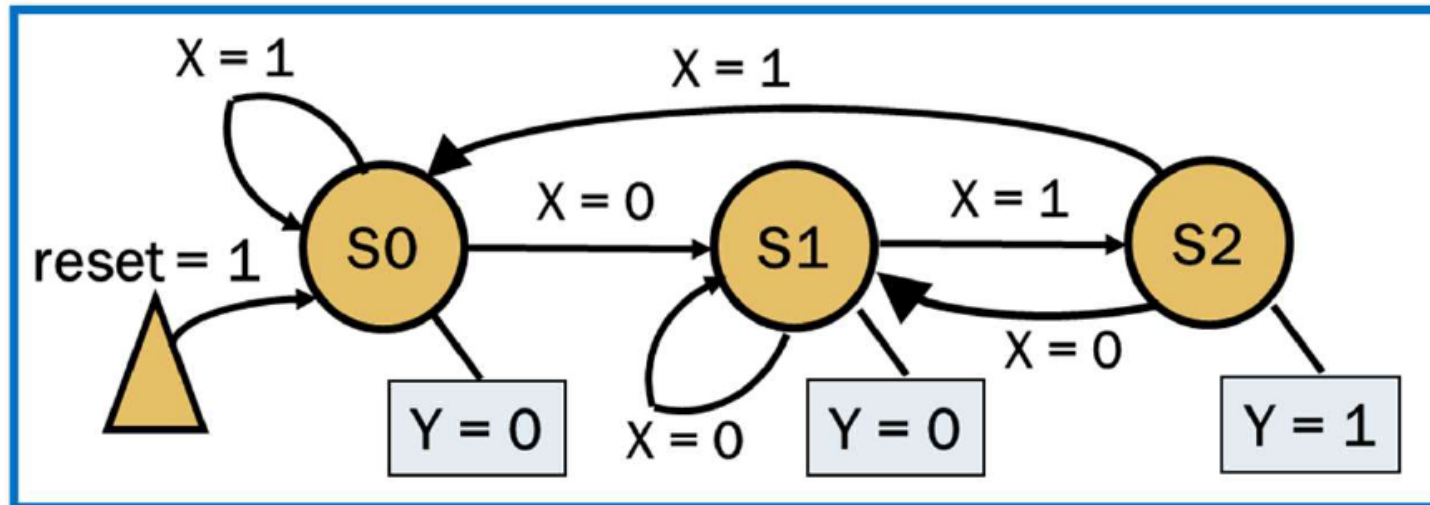
## Παράδειγμα – Ανίχνευση ακολουθίας 01 - Moore



# VHDL – Finite State Machines

## Παράδειγμα – Ανίχνευση ακολουθίας 01 - Moore

```
library IEEE;  
use IEEE.STD_LOGIC_1164.ALL;
```

```
entity PATTERN_FSM is  
  Port ( CLK : in STD_LOGIC;  
        RESET : in STD_LOGIC;  
        X : in STD_LOGIC;  
        Y : out STD_LOGIC);  
end PATTERN_FSM;
```

```
architecture Behavioral of PATTERN_FSM is
```

```
-- state definition
```

```
type FSM_states is (S0, S1, S2);
```

```
-- internal signals
```

```
signal current_state, next_state: FSM_states;
```

```
signal X_in : STD_LOGIC; -- Only when there is an INREG
```

**ΛΟΓΙΚΗ για  
RESET**



```
begin
```

```
-- Optional for synchronization. RESET case
```

```
INREG: process (CLK)
```

```
begin
```

```
if (CLK = '1' and CLK'event) then
```

```
  if (RESET = '1') then X_in <= '1'; -- to trap state S0 during reset
```

```
  else X_in <= X;
```

```
  end if;
```

```
end if;
```

```
end process;
```

```
-- Common process for all FSMs to create state register
```

```
SYNC: process (CLK)
```

```
begin
```

```
if (CLK = '1' and CLK'event) then
```

```
  if (RESET = '1') then current_state <= S0;
```

```
  else current_state <= next_state;
```

```
  end if;
```

```
end if;
```

```
end process;
```

# VHDL – Finite State Machines

## Παράδειγμα – Ανίχνευση ακολουθίας 01 - Moore

```
-- Process to create next state logic and output logic
ASYNC: process (current_state, X_in) -- Moore
begin
-- FSM next state and output initialization
next_state <= S0;
Y <= '0';
case current_state is
when S0 =>
if (X_in = '0') then next_state <= S1;
else next_state <= S0;
end if;
when S1 =>
if (X_in = '1') then next_state <= S2;
else next_state <= S1;
end if;
```

Αρχική τιμή  
οι τιμές  
Reset

ΛΟΓΙΚΗ για  
ΕΠΟΜΕΝΗ ΚΑΤΑΣΤΑΣΗ

```
when S2 => Y <= '1';
if (X_in = '0') then next_state <= S1;
else next_state <= S0;
end if;
-- fail-safe behavior
when others => next_state <= S0;
end case;
end process;

end Behavioral;
```


ΛΟΓΙΚΗ για  
ΕΞΟΔΟ

# VHDL – Finite State Machines

## Παράδειγμα – Ανίχνευση ακολουθίας 01 – Moore - RTL


Λογική Επόμενης Κατάστασης  
Συνδυαστικό

Λογική Εξόδου  
Συνδυαστικό

 


# VHDL – Finite State Machines
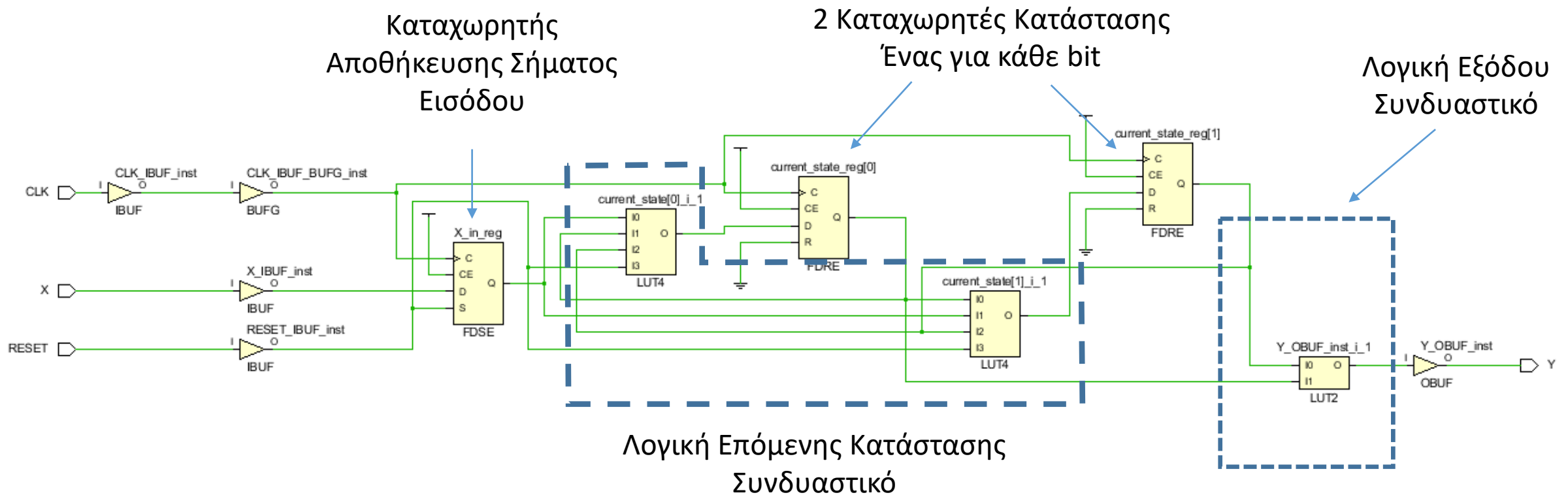
## Παράδειγμα – Ανίχνευση ακολουθίας 01 – Moore - Synthesis



# VHDL – Finite State Machines
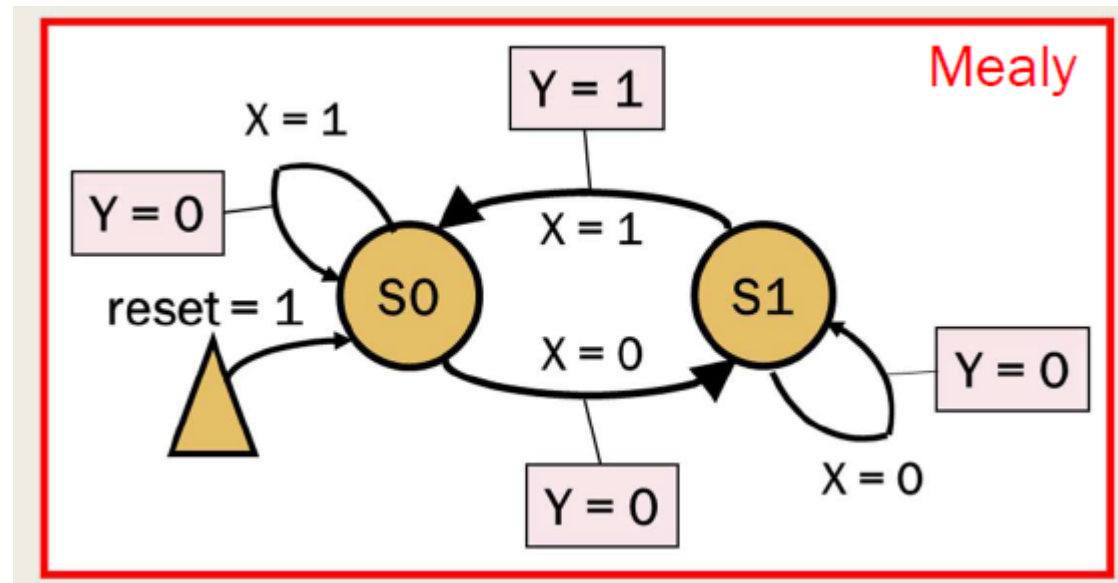
## Παράδειγμα – Ανίχνευση ακολουθίας 01 - Mealy





# VHDL – Finite State Machines

## Παράδειγμα – Ανίχνευση ακολουθίας 01 - Moore

```
library IEEE;  
use IEEE.STD_LOGIC_1164.ALL;
```

```
entity PATTERN_FSM is  
  Port ( CLK : in STD_LOGIC;  
        RESET : in STD_LOGIC;  
        X : in STD_LOGIC;  
        Y : out STD_LOGIC);  
end PATTERN_FSM;
```

```
architecture Behavioral of PATTERN_FSM is
```

```
-- state definition
```

```
  type FSM_states is (S0, S1);
```

```
-- internal signals
```

```
  signal current_state, next_state: FSM_states;  
  signal X_in : STD_LOGIC; -- Only when there is an INREG
```

```
begin
```

```
-- Optional for synchronization
```

```
  INREG: process (CLK)
```

```
  begin
```

```
    if (CLK = '1' and CLK'event) then
```

```
      if (RESET = '1') then X_in <= '1'; -- to trap state S0 during reset
```

```
      else X_in <= X;
```

```
      end if;
```

```
    end if;
```

```
  end process;
```

```
-- Common process for all FSMs to create state register
```

```
  SYNC: process (CLK)
```

```
  begin
```

```
    if (CLK = '1' and CLK'event) then
```

```
      if (RESET = '1') then current_state <= S0;
```

```
      else current_state <= next_state;
```

```
      end if;
```

```
    end if;
```

```
  end process;
```

# VHDL – Finite State Machines

## Παράδειγμα – Ανίχνευση ακολουθίας 01 - Mealy

```
-- Process to create next state logic and output logic
ASYNC: process (current_state, X_in) -- Moore
begin
-- FSM next state and output initialization
next_state <= S0;
Y <= '0';
case current_state is
when S0 =>
if (X_in = '0') then next_state <= S1;
else next_state <= S0;
end if;
when S1 =>
if (X_in = '1') then
next_state <= S0;
Y <= '1';
else next_state <= S1;
end if;
-- fail-safe behavior
when others => next_state <= S0;
end case;
end process;
end Behavioral;
```


**ΛΟΓΙΚΗ για  
ΕΞΟΔΟ**



# VHDL – Finite State Machines

Παράδειγμα – Ανίχνευση ακολουθίας 01 – Moore – Πίνακας Αληθείας

$S_{old}$	$S_{old}(1)$	$S_{old}(0)$	$X_{in}$	$S_{new}(1)$	$S_{new}(0)$	$S_{new}$	$Y$
$S_0$	0	0	0	0	1	$S_1$	0
$S_1$	0	1	0	0	1	$S_1$	0
$S_2$	1	0	0	0	1	$S_1$	0
$S_3$	1	1	0	0	0	$S_0$	0
$S_0$	0	0	1	0	0	$S_0$	0
$S_1$	0	1	1	1	0	$S_2$	1
$S_2$	1	0	1	0	0	$S_0$	0
$S_3$	1	1	1	0	0	$S_0$	0

 

# VHDL – Finite State Machines

## Παράδειγμα – Ανίχνευση ακολουθίας 01 – Moore – Πίνακες Αληθείας

Πίνακες KARNAUGH

		$S_{new}(1)$	
$S_{old} \backslash X_{in}$		0	1
00		0	0
01		0	1
11		0	0
10		0	0

		$S_{new}(0)$	
$S_{old} \backslash X_{in}$		0	1
00		1	0
01		1	0
11		0	0
10		1	0


		Y	
$S_{old} \backslash X_{in}$		0	1
00		0	0
01		0	1
11		0	0
10		0	0

$$\begin{aligned} S_{new}(1) &= S_{old}(1)' S_{old}(0) X_{in} \\ S_{new}(0) &= S_{old}(1)' X_{in}' + S_{old}(1) S_{old}(0)' X_{in}' \\ Y &= S_{old}(1) S_{old}(0)' X_{in} \end{aligned}$$


# VHDL – Finite State Machines

## Παράδειγμα – Ανίχνευση ακολουθίας 01 – Moore – Πίνακες Αληθείας

$X_{in}=S$	Out	$S1_{new}$
1	10	$S_2$
0	01	$S_1$

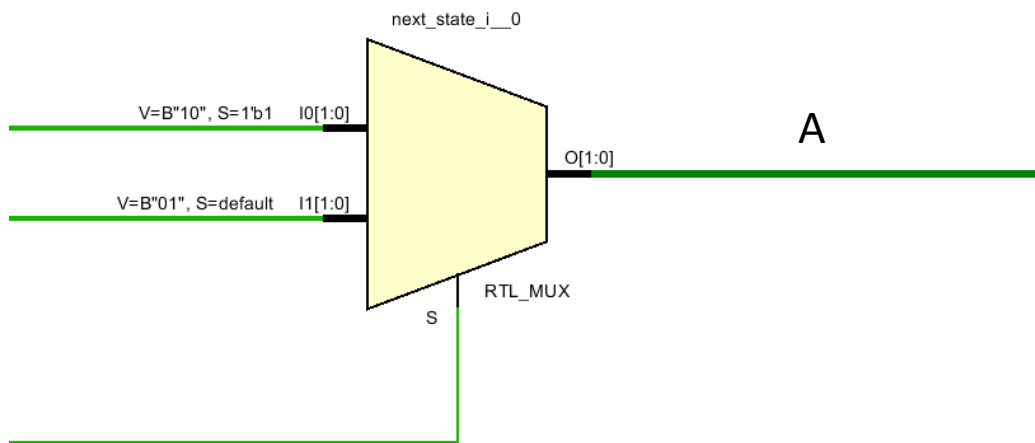

$X_{in}=S$	Out	$S1_{new}$
0	1	$S_1$
1	0	$S_0$

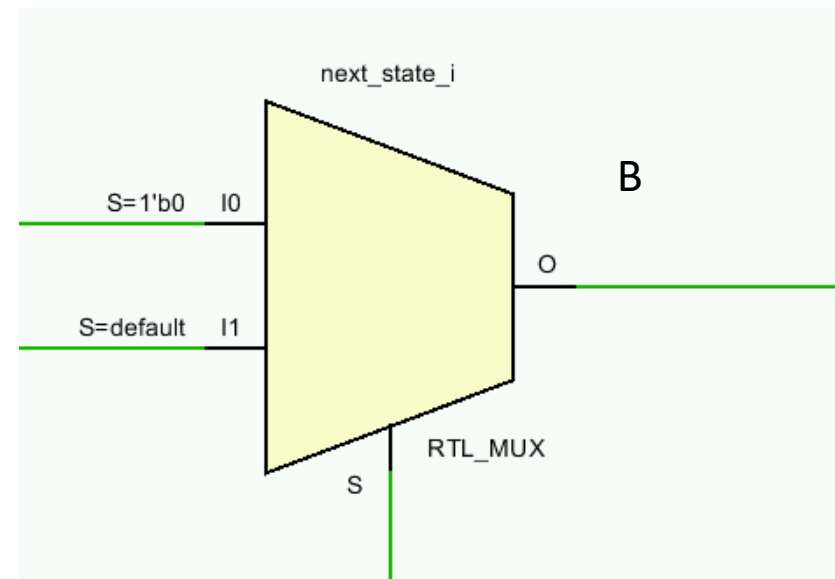

# VHDL – Finite State Machines


## Παράδειγμα – Ανίχνευση ακολουθίας 01 – Moore – Πίνακας Αληθείας

$X_{in}=S$	Out	$S_{new}$
1	10	$S_2$
0	01	$S_1$

A

$X_{in}=S$	Out	$S_{new}$
0	01	$S_1$
1	00	$S_0$

B

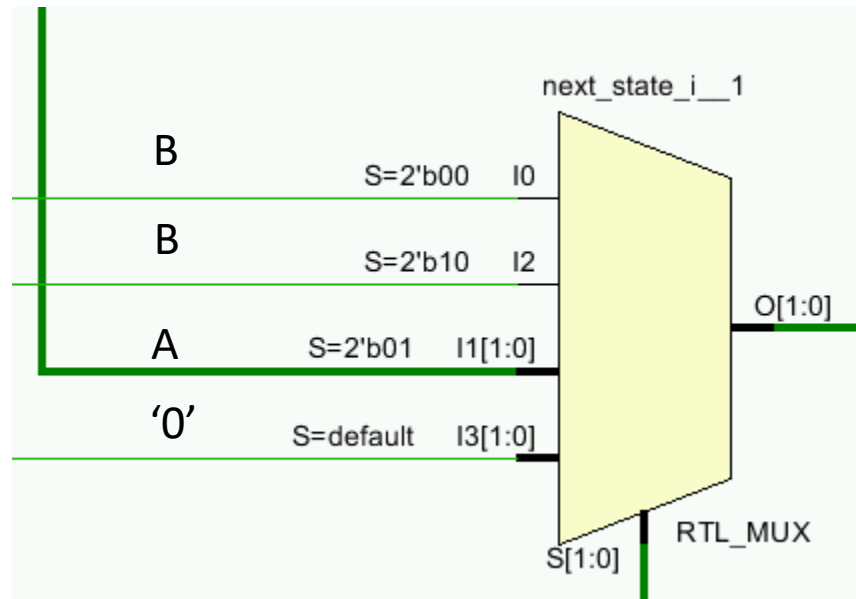

$S_{old}$	$X_{in}$	$S_{new}$
00(0)	0	$S_1$
01(1)	0	$S_1$
10(2)	0	$S_1$
11(X)	0	$S_0$
00(0)	1	$S_0$
01(1)	1	$S_2$
10(2)	1	$S_0$
11(X)	1	$S_0$

# Διακόπτες και αποκλυδωνισμός

- Οι διακόπτες (switches) και οι πιεστικοί διακόπτες (push-buttons) υποφέρουν από κλυδωνισμό επαφής
- Χρειάζονται περίπου 10ms να σταθεροποιηθούν
  - Χρειάζεται να αποκλυδωνίσουμε (debounce) για να αποφύγουμε τις ψεύτικες ενεργοποιήσεις
  - Χρησιμοποιούμε ένα διακόπτη μίας θέσης
  - Κάνουμε δειγματοληψία στην είσοδο σε διαστήματα μεγαλύτερα από το χρόνο κλυδωνισμού (>10ms)  
Στην κάρτα του εργαστηρίου σημαίνει 100000 χτύπους του ρολογιού.
  - Αναζητούμε δύο διαδοχικά δείγματα με την ίδια τιμή

# VHDL - Αποκλυδωνισμός

## Παράδειγμα (1/2)

```
library ieee; use ieee.std_logic_1164.all;  
entity debouncer is  
port ( clk, reset : in std_logic; -- clk frequency = 100MHz  
      pb : in std_logic;  
      pb_debounced : out std_logic );  
end entity debouncer;
```

```
architecture rtl of debouncer is
```

```
signal count1000000 : integer range 0 to 999999;  
signal clk_100Hz : std_logic; --10ms  
signal pb_sampled : std_logic;
```

```
begin
```



# VHDL - Αποκλιδωνισμός

## Παράδειγμα (2/2)

```
div_100Hz : process (clk, reset) is
begin
if reset = '1' then
    clk_100Hz <= '0';
    count500000 <= 0;
elsif rising_edge(clk) then
    if count1000000 = 999999 then
        count1000000 <= 0;
        clk_100Hz <= '1';
    else
        count1000000 <= count1000000 + 1;
        clk_100Hz <= '0';
    end if;
end if;
end process div_100Hz;
```

```
debounce_pb : process (clk) is
begin
if rising_edge(clk) then
    if clk_100Hz = '1' then
        if pb = pb_sampled then
            pb_debounced <= pb;
        end if;
        pb_sampled <= pb;
    end if;
end if;

end process debounce_pb;

end architecture rtl;
```

# Περίληψη

Harris: Παράγραφοι 3.4, 3.5 και 4.6

Ashenden: Παράγραφοι 4.3 και 4.4

Επίσης οι σύνδεσμοι:

<https://stackoverflow.com/questions/21351273/is-it-possible-to-synthesize-vhdl-code-with-variable-in-it>

Assert και Report: <https://insights.sigasi.com/tech/vhdl-assert-and-report/>